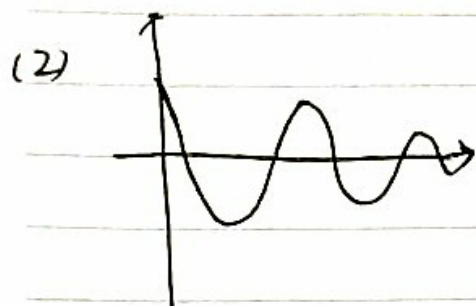


练习 12.1

$$(1) \omega_0 = \frac{1}{\sqrt{LC}} = 10^7 \text{ Hz}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2} \times 10^7 \text{ Hz}$$

$\therefore \alpha < \omega_0$ 欠阻尼



(3) 图示二阶网络衰减的包络线与前图电路的纵坐标为 $\frac{\omega_0}{\omega}$ 倍

练习 12.4

$$\alpha = \frac{R_1 + R_2}{2L} = 1.5 \times 10^7 \text{ Hz} \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2 \times 10^7 \text{ Hz}$$

$\therefore \omega_0 < \alpha$ 过阻尼

练习 12.8

(a) 特征方程: $\frac{1}{RC} \frac{dv}{dt} + \frac{d^2v}{dt^2} + \frac{R}{L} v = 0$

$$s^2 + \frac{1}{RC}s + \frac{R}{L} = 0$$

$$\therefore \alpha = \frac{1}{2RC} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

(b) $\omega_0 = \frac{1}{\sqrt{LC}} \quad \alpha = \frac{R}{2L}$

问题 12.6

(1) $t \leq 0$ 时 $i_L = 0, V_C = 2V$
 $t > 0$ 时: $\frac{dV}{dt} + 4 \frac{1}{C} V = 0$
 $\omega_0 = \frac{1}{\sqrt{LC}} = 10$

$$V_C(t) = 2 \cos 10t$$

$$i_L(t) = 20 \sin 10t$$